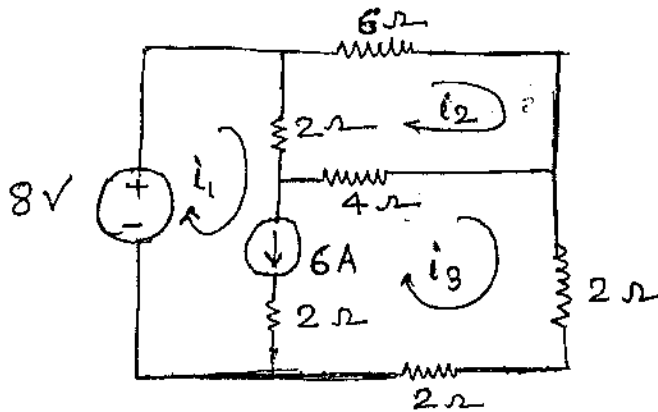


- N.B. :** (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of six questions.
 (3) Figures to the right indicate full marks.
 (4) Assume suitable data if required.


1. Solve the following :-

20


(a) For given network, find the current i_1 , i_2 and i_3 .



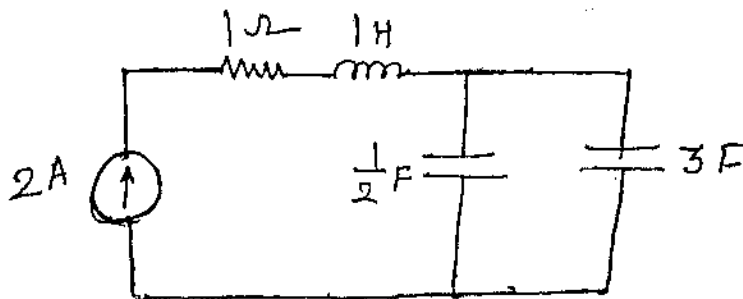(b) Draw the dual network of the circuit shown in figure



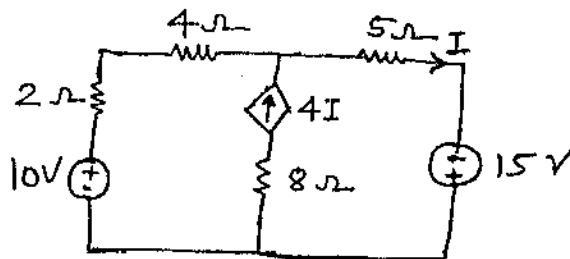
- (c) Find condition of symmetry in h-parameter and ABCD parameter.
 (d) Find the current in all branches of network shown in figure and voltage across current source.




(e) Using relation $y = z^{-1}$, show that $|z| = \frac{1}{2} \left(\frac{z_{22}}{y_{11}} + \frac{z_{11}}{y_{22}} \right)$.

2. (a) Find V_x by using superposition theorem for network shown in figure -

10

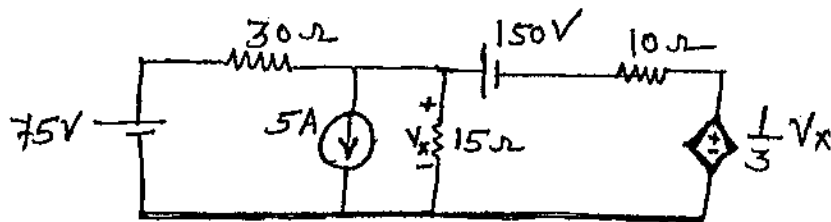


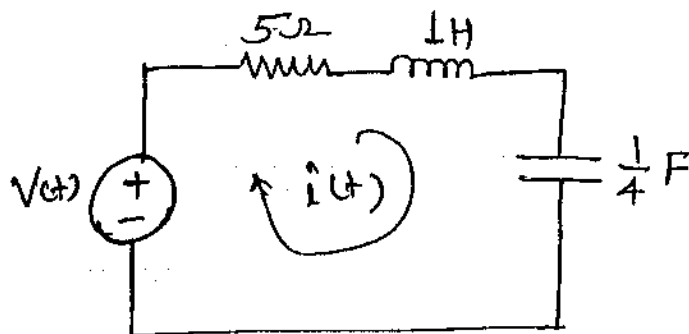- (b) Determine the current $i(t)$ in a series RLC circuit shown in figure, when each of the following forces (voltages) is applied (i) Ramp Voltage $12r(t-2)$ and (ii) Step Voltage $3u(t-2)$. Assume that the circuit was initially relaxed. Use Laplace transform method.




3. (a) Draw the Thevenin's equivalent network for circuit shown in figure below -


10

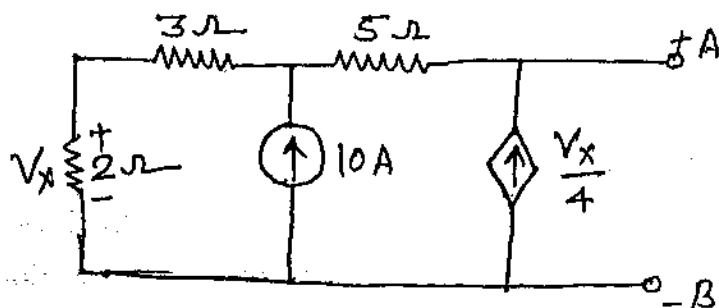

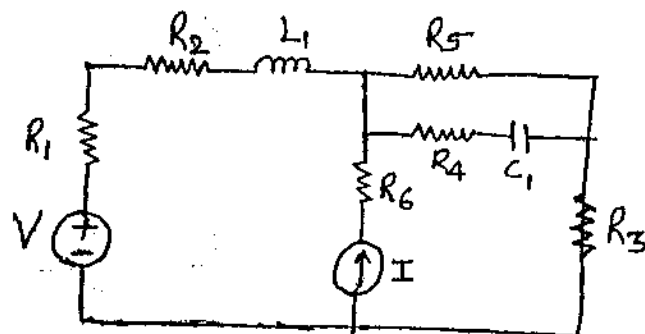
- (b) For the circuit shown in figure, write incidence matrix, fundamental cutset matrix and fundamental tieset matrix.



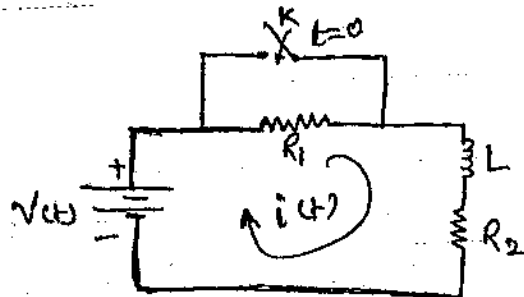
4. (a) In the given circuit, switch 'K' is closed at time $t = 0$, the steady state condition having reached previously. Obtain an expression for the current in the circuit at any time t . If $R_1 = R_2 = 100$ ohms, $V = 10$ volts and $L = 1$ henry, calculate at time $t = 5$ millisecond - (i) current i (ii) voltage drop across R_2 and (iii) voltage across L . 10



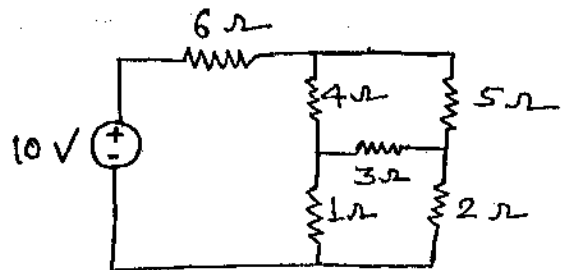
- (b) For the network shown in figure, draw the linear graph and write equilibrium 10 equation for KVL. Also find the loop currents.



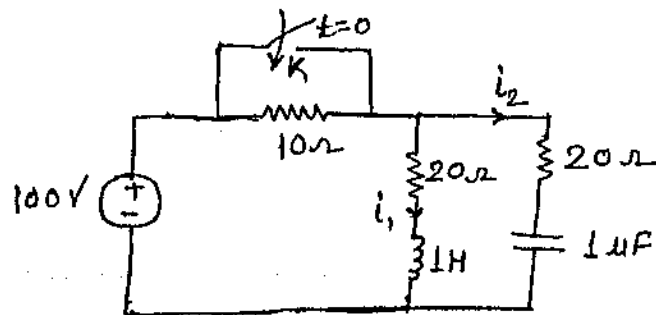
5. (a) Determine $V_c(0^+)$, $i_1(0^+)$, $\frac{di_1}{dt}(0^+)$ and $\frac{d^2i_2}{dt^2}(0^+)$ for the circuit shown in figure. 10
Assume zero initial conditions.



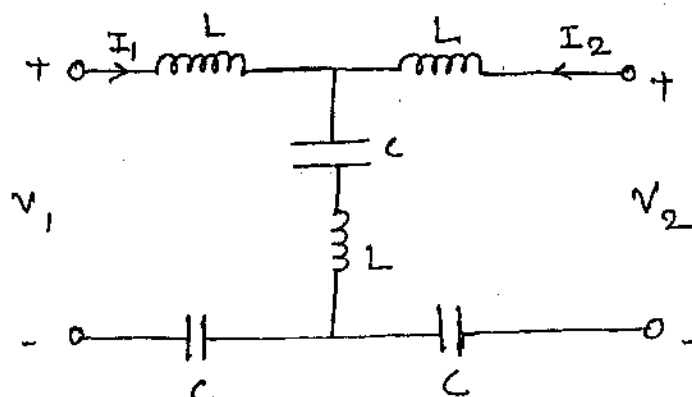- (b) Find z parameter by using interconnection relation. 10




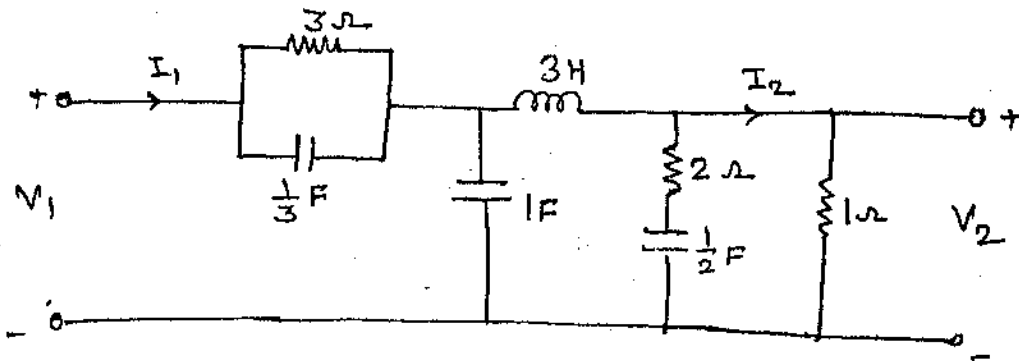6. (a) Determine the voltage ratio $\frac{V_2}{V_1}$, current ratio $\frac{I_2}{I_1}$, transfer impedance $\frac{V_2}{I_1}$ and driving point impedance $\frac{V_1}{I_1}$ for the network shown in figure -



- (b) Find z and h parameter for the network shown in figure -

10

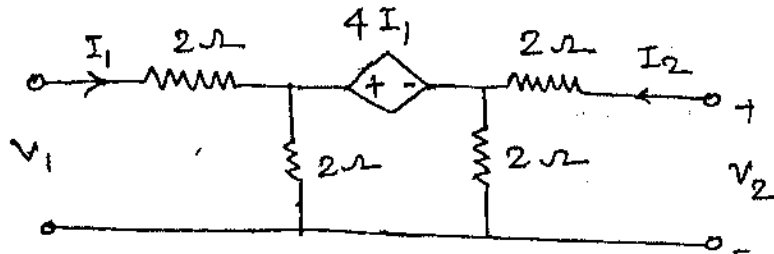

7. (a) (i) Test whether the given polynomial is Hurwitz or not

5

$$F(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$

- (ii) Check whether $F(s) = \frac{s+2}{s^2+3s+2}$ is positive real function.

5

- (b) Synthesize the following functions :-

10

(i) $Z(s) = \frac{s^3 + 12s^2 + 32s}{s^2 + 7s + 6}$ for Cauer II form

(ii) $Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$ for Foster II form.